

## Decoder Circuit using IC 7447


We already published the article about [3 to 8 decoder circuit using basic logic gates](#)(AND, OR, NOT Gates) with Seven Segment display as well as LEDs. That circuit was very complex but that gives you a good knowledge about Decoder Circuit. In this article, we are going to know **BCD to Seven Segment Display Decoder**(using a single IC) with examples and circuit diagrams.

BCD means **Binary Coded Decimal**. We can represent each of the decimal numbers by its four-bit binary numbers.

To drive a Seven Segment Display we need BCD to Seven Segment Display Decoder circuit. So here we used an **IC 74LS47** for this work.

So before making the circuit let's know about the IC 74LS47.

### Pin Diagram of IC 74LS47 :

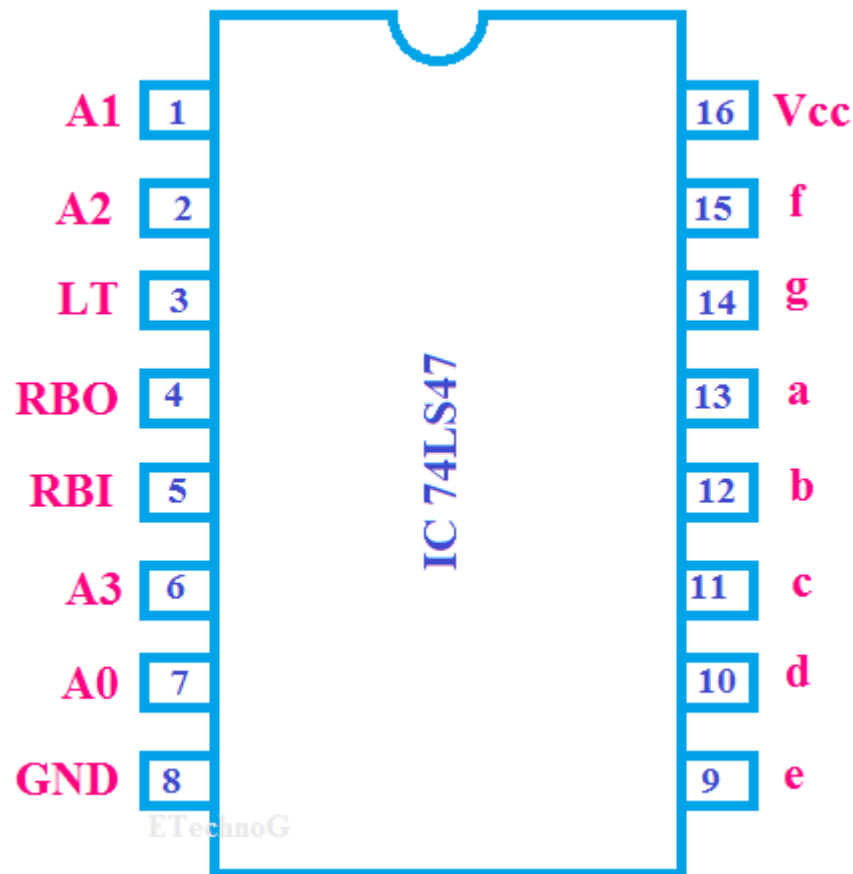

- A0, A1, A2, A3 are the BCD input pins.
- LT - for display test
- RBO, RBI is the Ripple blanking output and Ripple blanking Input pins respectively.
- a, b, c, d, e, f, g are the outputs for seven segment display.

Now let's make the circuit with a Common Anode Seven Segment Display,

We have four pins to give BCD inputs so we can display from 0 to 15 numbers but we need two seven segment display. In the below circuit diagram one seven segment display is used so here 0 to 9 numbers can be shown.

The **truth table** is given below for the circuit,

INPUTS						OUTPUTS								Decimal Number show in display
LT	RBO	A3	A2	A1	A0	a	b	c	d	e	f	g		
0	0	0	0	0	0	1	1	1	1	1	1	0		
0	0	0	0	0	1	0	1	1	0	0	0	0		
0	0	0	0	1	0	1	1	0	1	1	0	1		
0	0	0	0	1	1	1	1	1	1	0	0	1		
0	0	0	1	0	0	0	1	1	0	0	1	1		
0	0	0	1	0	1	1	0	1	1	0	1	1		
0	0	0	1	1	0	1	0	1	1	1	1	1		
0	0	0	1	1	1	1	1	1	0	0	0	0		
0	0	1	0	0	0	1	1	1	1	1	1	1		
0	0	1	0	0	1	1	1	1	1	0	1	1		

Circuit diagram of Decoder Circuit:

